

# Microelectronics and Integrated Circuit, Opamp design

Daniel Toribio & Andrés Navarro

The sizes of the transistors have been obtained with these computations:

CIM, opamp design

$$SR = \frac{I_7}{C_c}$$


$$SR \geq 10V/\mu s$$

$$C_c \geq 0,22 C_L \Big|_{C_L = 4pF} = 0,88pF \Rightarrow [1pF = C_c] \Rightarrow I_7 = SR \cdot C_c = 100\mu A \Rightarrow I_7 = 150\mu A$$

$$P = V_{DD} (I_{bias} + I_7 + I_6) \leq 0,5mW$$

$$I_{bias} = I_7 = I_6 = 150\mu A$$


simplifies the circuit

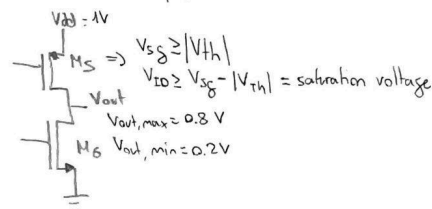

$$I_{D5} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_5 (V_{SDS,sat})^2$$

$$\left(\frac{W}{L}\right)_5 = \frac{2 \cdot I_{D5}}{\mu_p C_{ox} V_{SDS,sat}^2} = 166,67 \Rightarrow \left[\left(\frac{W}{L}\right)_5 = 170\right]$$
 
$$I_{D6} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_6 \cdot V_{DS,sat}^2 \Rightarrow \left(\frac{W}{L}\right)_6 = 83,3 \Rightarrow \left[\left(\frac{W}{L}\right)_6 = 90\right] \Rightarrow \left[\left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_8 = \left(\frac{W}{L}\right)_6 = 90\right]$$



$$0,6V = V_{GS2} + V_{DS,sat2} \Rightarrow V_{GS2} = 0,6 - 0,2 = 0,4V$$

$$V_{GS2} \geq V_{thn} = 0,3V$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{thn})^2$$


$$\left(\frac{W}{L}\right)_2 = \frac{2 \cdot I_{D2}}{\mu_n C_{ox} (V_{GS2} - V_{thn})^2} = \frac{2 \cdot 75}{90(0,4 - 0,3)^2} = 166,67$$

$$\Rightarrow \left[\left(\frac{W}{L}\right)_2 = 170 = \left(\frac{W}{L}\right)_1\right]$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 3 \left(\frac{W}{L}\right)_1 = 510$$

$$@50nm \Rightarrow L = 200nm \Rightarrow \begin{cases} W_1 = W_2 = 34\mu m & W_5 = 34\mu m \\ W_3 = W_4 = 102\mu m & W_6 = W_7 = W_8 = 18\mu m \end{cases}$$

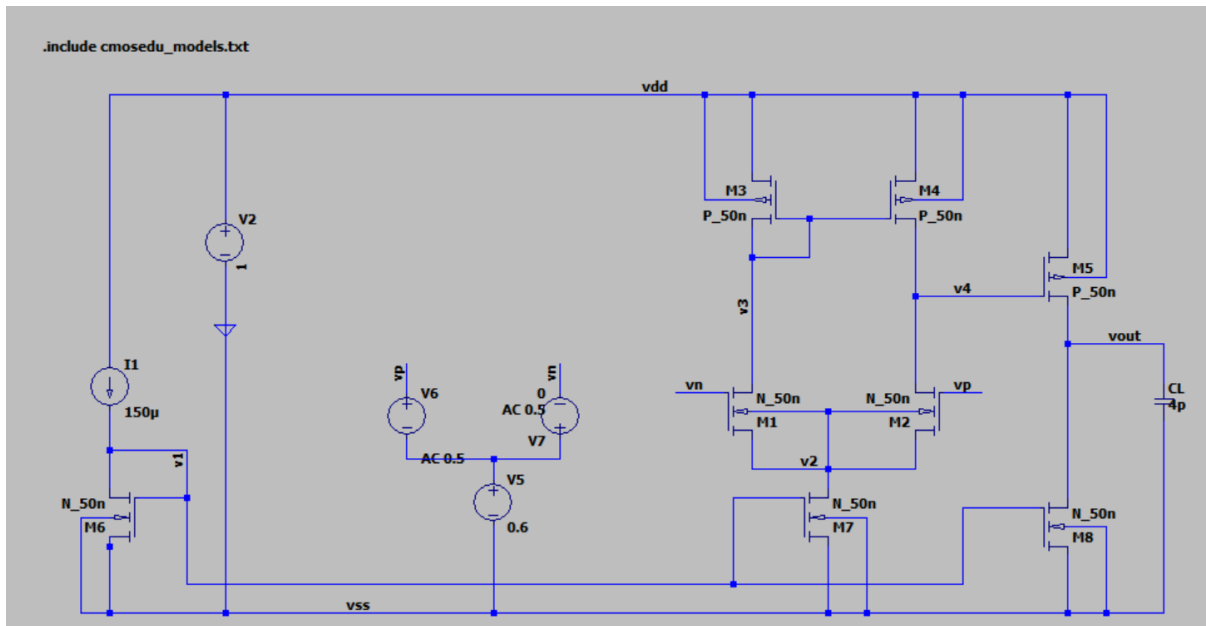This is the circuit we are going to use in the simulations:



After using these values in LTSpice we have seen that the output voltage is out of the range of the desired ones, which were between 0.2V and 0.8V.

### --- Operating Point ---

|           |           |         |
|-----------|-----------|---------|
| V(vdd) :  | 1         | voltage |
| V(vout) : | 0.0137487 | voltage |

We can see that the transistor 8 is not saturated:

|          |              |                |
|----------|--------------|----------------|
| Id(M8) : | -3.00576e-05 | device current |
|----------|--------------|----------------|

One possible way to solve this is to decrease the  $V_{sd}$ . To do that we have to increase  $I_d$  and to achieve that we can increase the  $W$  of transistor 7. We will use 120µm, the output voltage is now:

### --- Operating Point ---

|           |          |         |
|-----------|----------|---------|
| V(vdd) :  | 1        | voltage |
| V(vout) : | 0.490469 | voltage |

So we had to modify the  $W$  of transistor 7 from 18µm to 120µm.

After this modification we can measure the current flowing through M6, M7 y M8 and the sum of them will be multiplied by  $V_{DD}$  to obtain the power consumption, which is 650 µW.

The computations of the gain are the following ones:

$$gain \geq 50dB$$

$$gain = gain_1 \cdot gain_2$$

$$gain_1 = g_{m1} \cdot (r_{o2} \parallel r_{o4})$$


$$\left. \begin{aligned} g_{m1} &= \sqrt{2 \cdot \mu_n \cdot C_{ox} \left( \frac{W}{L} \right) \cdot I_D} = \sqrt{2 \cdot 90 \cdot 170 \cdot 75} = 1514 \mu A/V \\ r_{o2} &= \frac{1}{\lambda_n I_D} = \frac{1}{0,6 \cdot 75 \mu} = 22 k\Omega \\ r_{o4} &= \frac{1}{0,3 \cdot 75 \mu} = 44 k\Omega \end{aligned} \right\} r_{o2} \parallel r_{o4} = 14,6 k\Omega \quad \left. \begin{aligned} & \\ & \end{aligned} \right\} gain_1 = 22 V/V$$

$$gain_2 = g_{m5} \cdot (r_{o5} \parallel r_{o6})$$

$$\left. \begin{aligned} g_{m5} &= \sqrt{2 \cdot 45 \cdot 100 \cdot 150} = 3674 \mu A/V \\ r_{o5} &= \frac{1}{0,3 \cdot 150 \mu A} = 22 k\Omega \\ r_{o6} &= \frac{1}{0,8 \cdot 150 \mu} = 11 k\Omega \end{aligned} \right\} r_{o5} \parallel r_{o6} = 7,3 k\Omega \quad \left. \begin{aligned} & \\ & \end{aligned} \right\} gain_2 = 26,8 V/V$$

$$gain = 22 \cdot 26,8 = 589,6 V/V \Rightarrow 20 \log(589,6) = 55 dB$$

After the AC simulation we obtain:

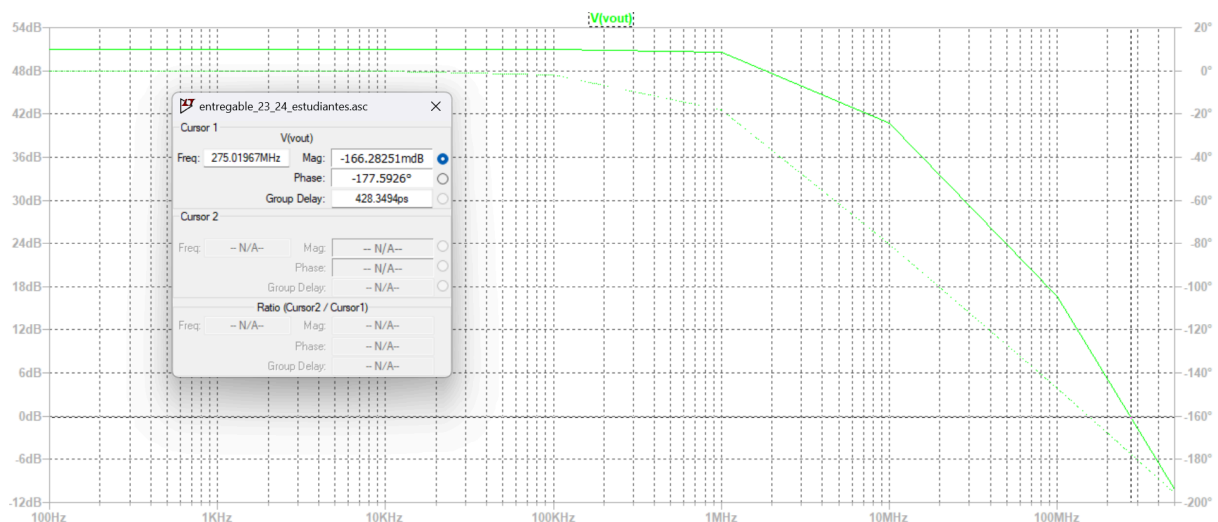

where we can see that the gain is 50dB which is similar to the one computed before. The GBW is 275 MHz.


For the stability we can see that the amplifier is stable because the phase at 0dB is 177.6 degrees, and the phase margin is  $180 - 177 = 3$  degrees, which is positive.

We can increase the phase margin by adding a resistor and a capacitor in series connecting v4 and vout. The capacitance of Cc was already computed, 1pF, and for the impedance of Rz we can use the formula of the statement:


$$R_Z = \frac{C_C + C_L}{C_C} \frac{1}{g_{m5}}$$

and we obtain that  $R_Z = 1360\Omega$

The resulting circuit is:

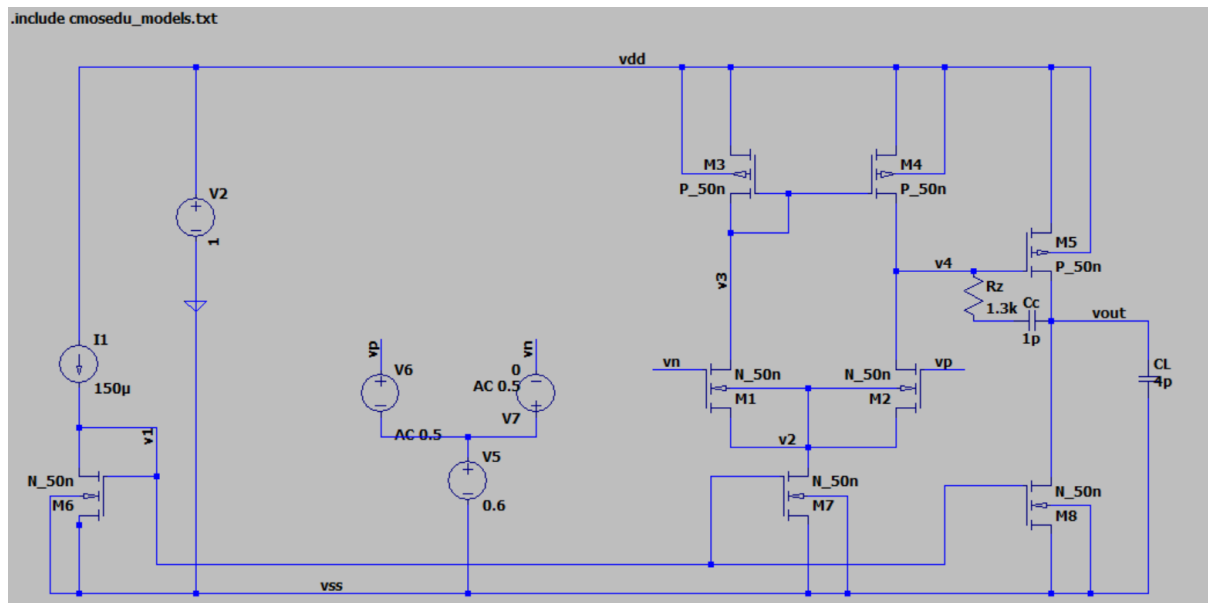


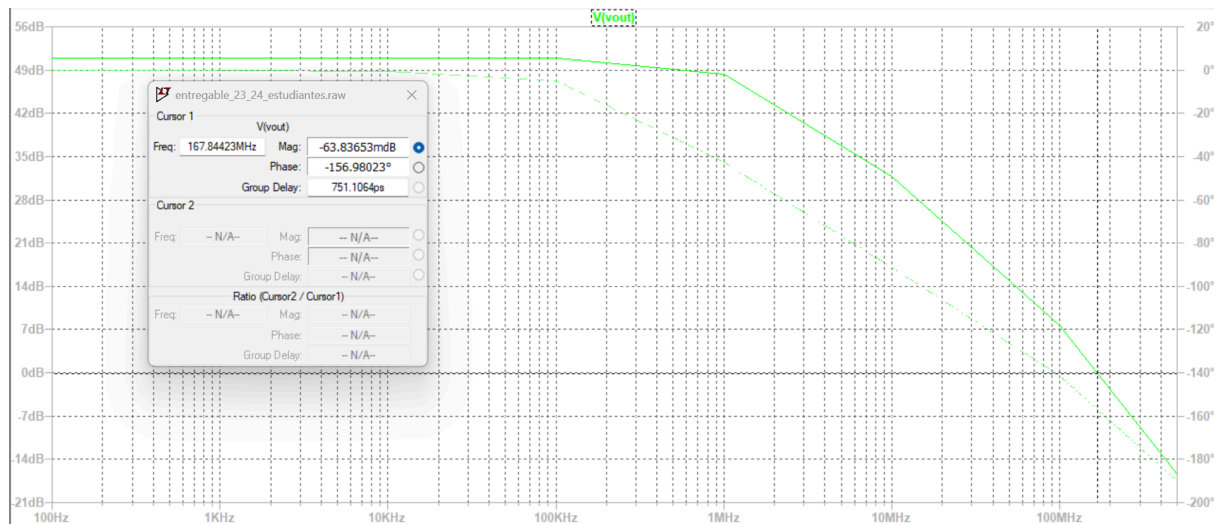We can see that now the phase at 0 db is:




so the phase margin is  $180 - 157 = 23$  degrees. We can see that we have increased the phase margin but the GBW is smaller, 168 MHz.

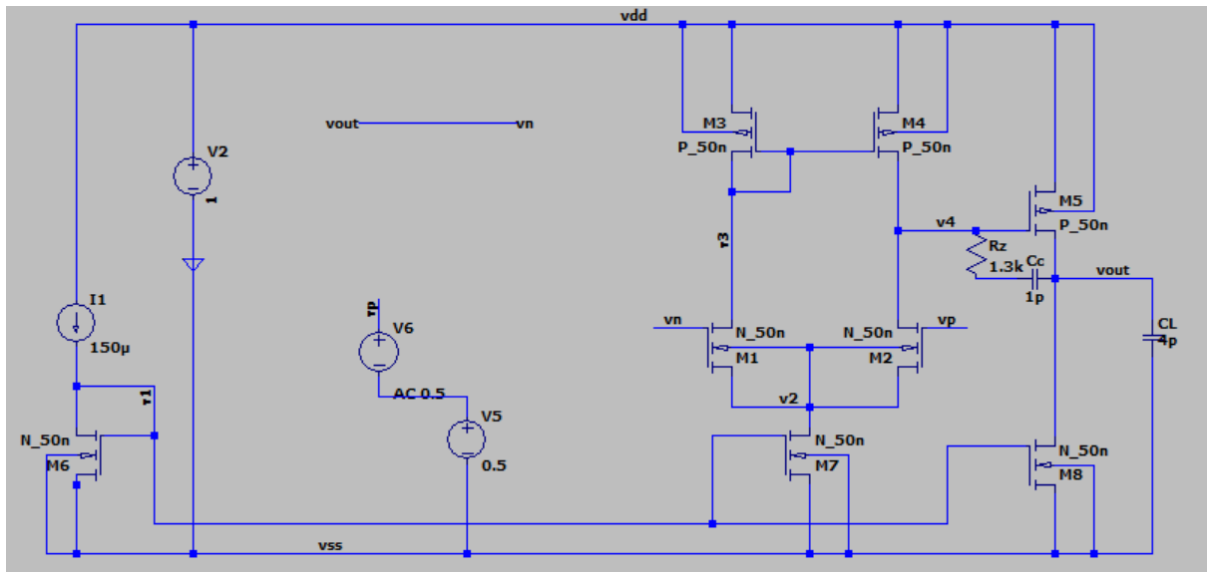For the third experiment we have to set up as a buffer the architecture. The resulting circuit is:




 We obtain this plot with a pulse between 0.5V and 0.6V with a frequency of 10 KHz :



and we can compute the slew rate is  $200345 \text{ mV/us} = 200.345 \text{ V/us}$  which is higher than the  $10\text{V/us}$  of the requirement.

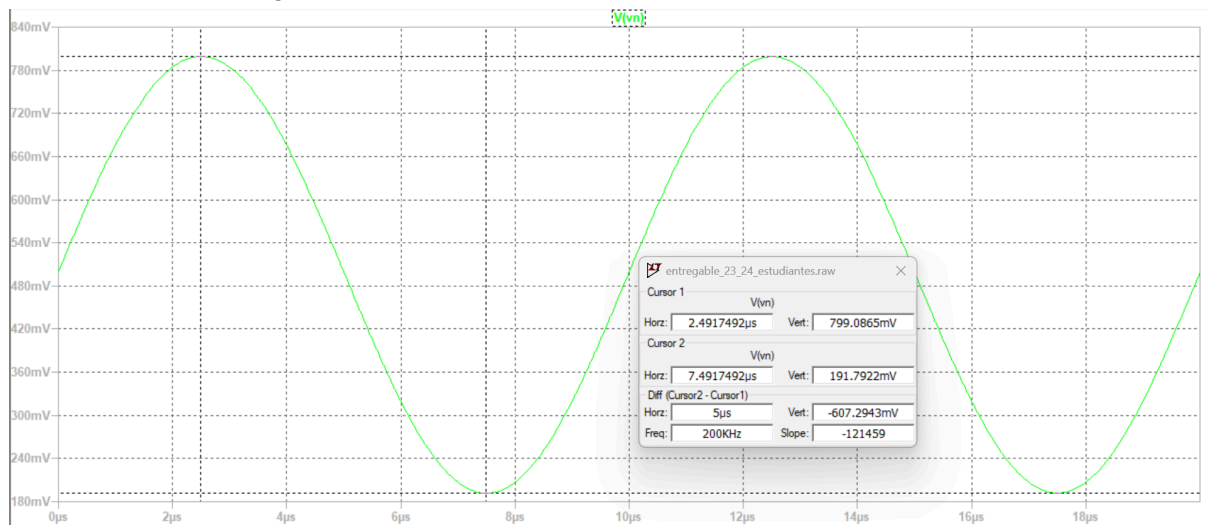This is the plot when we use a sinusoidal signal of 100 kHz, amplitude of 0.3 V and common-mode voltage of 0.5 V:




where we can see that the  $V_{out,min} = 0.19V$  and  $V_{out,max} = 0.8V$  which fulfills the requirements.

After carrying out the experiments we can answer the following questions:

- What is the purpose of the DC simulation performed?  
The purpose is to obtain the currents in the transistors and the voltage in the output. We are also able to compute the power consumption.
- What is the purpose of the AC simulation performed?  
With the AC simulation we can see the gain and the GBW. We can also compute the phase margin to see if the amplifier is stable.
- If the “hand-made” gain is not enough, how could you improve it?  
We can obtain a higher gain by increasing  $g_m$ , that can be increased by increasing the width of the transistor.
- If CL is reduced, how does GBW change?  
If CL is reduced the GBW increases.
- What is the purpose of CC and RZ?  
The purpose is to obtain a higher phase margin and make the operational amplifier more stable.
- How could you increase  $V_{out,max}$ ?  
We can increase  $V_{out,max}$  by increasing the total gain which is the product of  $g_{m1}$  and  $g_{m5}$ , as we can see in the computations, so by increasing the size of m1 or m5 we can increase the  $V_{out,max}$ .
- And decrease  $V_{out,min}$ ?  
We can decrease  $V_{out,min}$  by applying the same solution as in the previous question

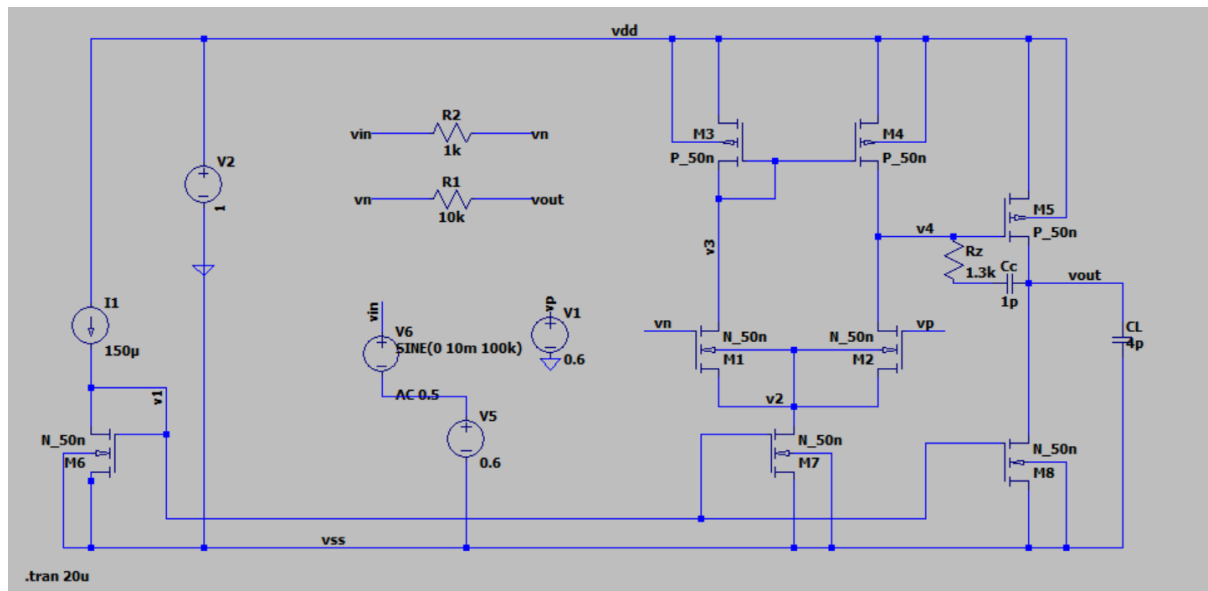Vin is a sinusoidal signal of 10-mV amplitude, 0.6 V common-mode voltage and frequency of 100kHz. What is the theoretical gain  $V_{out}/V_{in}$ ? Justify your answer. Run a transient simulation to verify whether the theoretical gain is accomplished or not. Copy the result of the simulation.



The plot displays two periodic signals over a time range from 0 to 18  $\mu\text{s}$ . The vertical axis represents voltage in millivolts (mV), ranging from 500 mV to 700 mV. The blue signal, labeled  $V(vin)$ , is a sine wave with an amplitude of approximately 20 mV, oscillating between 580 mV and 620 mV. The green signal, labeled  $V(vout)$ , is a sine wave with a larger amplitude of approximately 60 mV, oscillating between 500 mV and 700 mV. Both signals have a period of 10  $\mu\text{s}$ . The  $V(vout)$  signal is phase-shifted relative to  $V(vin)$ , starting at its peak at  $t = 0$  while  $V(vin)$  is at its average value.